 


CMOS INTEGRATED CIRCUIT DESIGN TECHNIQUES



Y. Triantouhas



CMOS Integrated Circuit Design Techniques


Overview



VLSI Systems
and Computer Architecture Lab

1. *Bi-stable circuits – Metastability*
2. *Latches – Flip-Flops*
3. *Pipelines*
4. *Mono-stable circuits*
5. *Clock generators – The PLL*
6. *Schmitt trigger circuits*
7. *Charge pumps*


Sequential Logic

 

Memory Elements

3


Bistable Circuits' Operating Principle

 


Memory Elements

4

Metastable & Stable Operating Points

 


 
A and B = stable operating points
C = metastable operating point



Memory Elements

5

Metastability

  

In case that signals D and $\overline{D}$ are making transitions almost concurrently with the clock signal CLK , then the following scenario is possible: the clock signal enters the memory state while the voltage level of both internal nodes $\overline{Q}$ and Q is close to the transition threshold of the two inverters. As a result the latch will arrive to its final state after a quite long time interval, while the logic level of this state depends on random factors, like the noise!



Memory Elements

6


Latches

Memory Elements


7

Multiplexer Based Latch


Negative Latch

 


Positive Latch

 

Latch: Level-sensitive circuit

 

Complementary (non overlapping) clock

 


Memory Elements


8

Latch Timing

Negative Latch

 

Positive Latch

 


Memory Elements

9

Controllable Feedback Latch

 A D-latch is sensitive to the level of the clock signal CLK. One level stands for the *transparent mode of operation* where the input data pass to the circuit output Q. The other level stands for the *memory mode of operation* where the latch output Q holds the last value of the D input before the transition of the clock from the transparency level to the memory level.




The feedback inverter can be designed with the $k_{p,n}$ factor of the transistors to be small. In that case the following pass-gate can be eliminated.

Memory Elements

10


Latch Timing Characteristics

 

Memory Elements

11

Feedback D Latch

 

Memory Elements


12

Flip Flops

Memory Elements


13

Master-Slave D Flip-Flop

 

A Flip-Flop is an *edge-triggered* memory element. It is sensitive to a clock edge and not to a clock level. Only at this specific edge the input data pass to the output.

 2 cascaded Latches
with complementary clocks





Static Flip-Flop

Memory Elements

14

Master-Slave D Flip-Flop Operation

 
 


Memory Elements

15

Multiplexer Based D Flip-Flop


Static Flip-Flop

  

Memory Elements

16


D Flip-Flop Timing Characteristics

 

Memory Elements

17


D Flip-Flop Timing

 

Memory Elements

18


Setup and Hold Times

 

19

Two-Phase C²MOS D Flip-Flop

Dynamic Flip-Flop

 

Memory Elements

20

Non-Overlapping Phases Generation

The diagram illustrates a circuit for generating two non-overlapping clock phases, Φ_1 and Φ_2 , from a single input clock signal labeled CLK. The CLK signal is split into two parallel paths. The upper path consists of an inverter followed by an OR gate. The lower path consists of an inverter followed by an OR gate. The outputs of these two OR gates are Φ_1 and Φ_2 respectively. The circuit is designed such that Φ_1 and Φ_2 are non-overlapping, meaning they are never both high at the same time.

Memory Elements

21



21

Double Edge Triggered Flip-Flop

The diagram illustrates a Double Edge Triggered Flip-Flop (DETFF) circuit. It consists of two dynamic latches and a cross-coupled output stage.

- Input D:** The data input signal, shown as a square wave.
- Active High Dynamic Latch:** A dashed red box highlights the top latch. It has two clock inputs (CLK) and one data input (D). The output of this latch is labeled **1**.
- Active Low Dynamic Latch:** A dashed blue box highlights the bottom latch. It has two clock inputs (CLK) and one data input (D). The output of this latch is labeled **1**.
- Output Stage:** The outputs of the two latches are connected to a cross-coupled output stage. The output of the top latch is connected to the input of the bottom latch, and the output of the bottom latch is connected to the input of the top latch. The output of the top latch is labeled **0** and the output of the bottom latch is labeled **1**.
- Power and Ground:** The circuit is powered by V_{DD} and grounded (Gnd).

Double Edge Triggered FF (DETFF)


Memory Elements

22



22

Pipelines I

 


$$T_{\min, \text{org}} = t_{c \rightarrow q} + (t_{p_{\text{add}}} + t_{p_{\text{abs}}} + t_{p_{\text{log}}}) + t_{\text{su}}$$

$$T_{\min, \text{pipe}} = t_{c \rightarrow q} + \max(t_{p_{\text{add}}}, t_{p_{\text{abs}}}, t_{p_{\text{log}}}) + t_{\text{su}}$$

in case that $t_{p_{\text{add}}} = t_{p_{\text{abs}}} = t_{p_{\text{log}}}$
 
$$\text{then } T_{\min, \text{pipe}} \cong \frac{T_{\min, \text{org}}}{3}$$





Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$



Memory Elements

23

Pipelines II

  

Memory Elements

24



Other Circuits



Memory Elements

25


Monostable Circuits

  

Memory Elements

26


Non-Stable Circuits

 

Ring Oscillator

$$f_{osc} = \frac{1}{n \cdot (t_{d0 \rightarrow 1} + t_{d1 \rightarrow 0})}$$

 $n = \# \text{ \beta \alpha \mu \iota \delta \omega \nu }$




Memory Elements

27

Clock Generation

Phase Locked Loops (PLLs)

 


- High frequency clock CLK generation from a low frequency reference clock $CLK_{\epsilon\xi}$

Memory Elements

28


Phase – Frequency Detector I

 

Memory Elements

29

Charge Pump and Filter II

 


Memory Elements


30

Voltage Controlled Oscillator (VCO) III

 Curve slope: $K_{VCO} = 2\pi \frac{f_{\max} - f_{\min}}{V_{\max} - V_{\min}}$




Current-Starved VCO

 

Memory Elements

31

Frequency Divider IV

 


Binary Counter

$$f = \frac{1}{T_{CLK}}$$

Memory Elements

32


Clock Distribution

 

Memory Elements

33


Grid Clock Distribution

 


Memory Elements

34


Central Clock Distribution

 

H-Tree Clock Distribution (I)

 


H-Tree Clock Distribution (II)

 


37

The Schmitt Trigger Circuit

 


38



Voltage Generators

 

MOS Positive Charge Pump

 

MOS Negative Charge Pump

  

*Charge Pump
with MOS Capacitors*



Memory Elements

41